

Verilog Summary

- ❑ The following slides briefly review the main points in Verilog Modeling
 - Verilog Variables
 - Verilog Modules
 - Verilog Dataflow Modeling
 - Verilog Operators
 - Verilog Multiplexed Datapaths
 - Verilog FSM-based Control


- ❑ Important! This course does not teach how to do Verilog modeling. These materials are used only to freshen up your mind.

References

- ❑ Official Standard:
IEEE Std 1364-2001
IEEE Standard Verilog Hardware Description
Language
<https://ieeexplore.ieee.org/stamp/stamp.jsp?tp=&arnumber=954909>
- ❑ Reference Guide:
Verilog 2001 Quick Reference Guide by Sutherland
HDL
https://sutherland-hdl.com/pdfs/verilog_2001_ref_guide.pdf
- ❑ Textbook:
Digital Design with RTL Design, VHDL, and Verilog by
Frank Vahid
<https://www.amazon.com/Digital-Design-RTL-VHDL-Verilog/dp/0470531088>


Verilog Variables

Wires and Regs

 

- ❑ A wire and a reg carry information around in a module
- ❑ A reg is a variable with storage
 - Assign value v at time t_1 , then the value will remain v for $t > t_1$ until reg is re-assigned
- ❑ A wire does not have storage, but it reflects the value of a driver
 - Assign value v at time t_1 , then the value is not valid for any other time than $t = t_1$


Wires and Regs

 

- ❑ A driver of a wire can be defined through expressions and multiple levels of hierarchy
- ❑ Eventually, all wires need a driver, otherwise their value is undefined

Value Levels

 
- ❑ Each wire can be at 1 of 4 logic levels



- ❑ Initially, variables start out at X
- ❑ X is contagious. E.g. logic operation $(0 \text{ or } X) = X$
- ❑ Z is contagious. E.g. logic operation $(1 \text{ and } Z) = X$


Driving Levels

- ❑ Ideally, a driver is a switch

 


Driving Levels

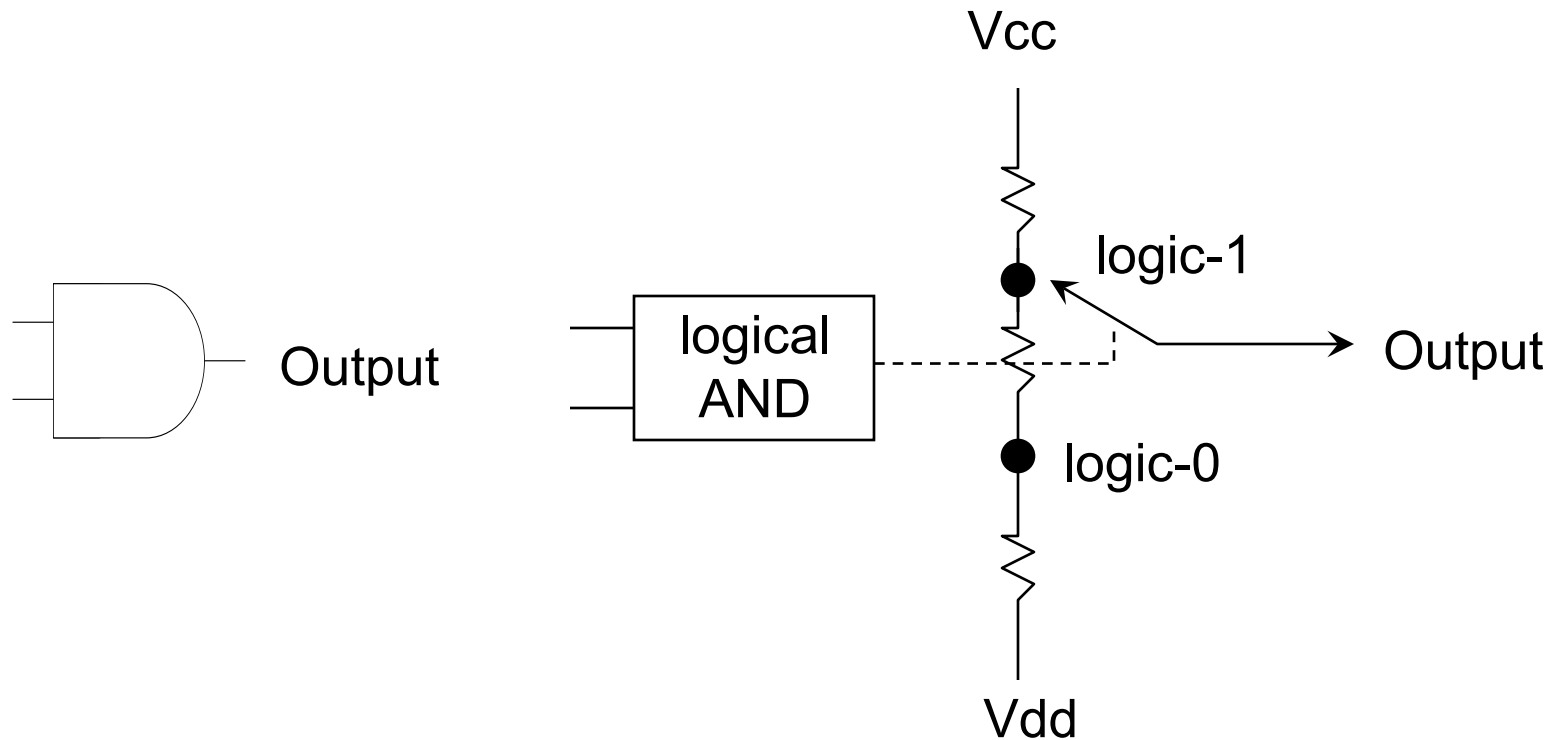- ❑ In reality, a driver has different strengths



Driving Levels

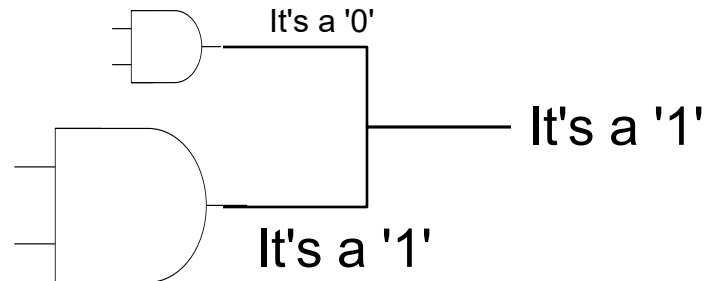- ❑ A driving level enables to simulate the electrical effect of different driving strengths
 - Can simulate the effect of signal contention
 - Can implement wired-AND and wired-OR
 - Can simulate tri-state buses
 - Can simulate large gates and small gates



- ❑ Verilog offers support for this type of simulation
 - We will stick to wire, reg and a single driving level for now

Vectors

```
wire [7:0] b,c; // two 8-bit vectors
                // msb is b[7] and c[7]
reg [0:20] a;    // 21-bit reg, msb is a[0]

b[7]           // bit 7 of the b bit-vector
c[6:5]         // bit 6 and 5 of the c bit-vector
a[3+:4]        // bit 3, 4, 5, 6 of a
```

Constants

<size>' **<base>** **<number>**

**number
of *bits***

b or B Binary
o or O Octal
h or H Hex
d or D Decimal

number in selected base
may use _ as a spacer
0-extended with 0 or 1 msb
x-extended with x msb
z-extended with z msb

For example ...

<size>' <base> <number>

6'b010_111	gives	010111
8'b0110	gives	00000110
8'b1110	gives	00001110
4'bx01	gives	xx01
16'H3AB	gives	0000001110101011
24	gives	0...0011000
5'O36	gives	11100
16'Hx	gives	xxxxxxxxxxxxxxxxxxxx
8'hz	gives	zzzzzzzz

Other Verilog Variables

- ❑ Besides reg, Verilog allows several other kinds of variables that have storage
- ❑ These are for test-benches, not for synthesis
 - integer (signed 32 bit)
 - time (unsigned 64 bit)
 - real (double precision)
 - realtime
- ❑ reg is unsigned; Verilog-2001 allows signed
 - signed reg a[3:0]; // 4-bit two's compl

Verilog Modules

Modules

```
module name (portlist) ;
```

```
    port declarations;
```

```
    parameter declarations;
```

```
    wire declarations;
```

```
    reg declarations;
```

```
    variable declarations;
```

```
    module instantiations;
```

```
    dataflow statements;
```

```
    always blocks;
```

```
    initial blocks;
```

```
    tasks and functions;
```

```
endmodule
```

Modules

```
module name(portlist);
```

```
port declarations;  
parameter declarations;
```

```
wire declarations;  
reg declarations;  
variable declarations;
```

```
module instantiations;  
dataflow statements;  
always blocks;  
initial blocks;
```

```
tasks and functions;
```

```
endmodule
```

```
- Direction of ports  
- Module variants  
(module muffin;  
    parameter banana_nut;)
```


Modules

```
module name(portlist);  
    port declarations;  
    parameter declarations;
```

```
    wire declarations;  
    reg declarations;  
    variable declarations;
```

```
    module instantiations;  
    dataflow statements;  
    always blocks;  
    initial blocks;
```

```
    tasks and functions;
```

```
endmodule
```

```
- local communication  
- local storage  
- local storage (testbench)
```



within the confines
of this module and this
level of the design hierarchy

Modules

```
module name (portlist) ;  
    port declarations;  
    parameter declarations;
```

```
    wire declarations;  
    reg declarations;  
    variable declarations;
```

```
    module instantiations;  
    dataflow statements;  
    always blocks;  
    initial blocks;
```

```
    tasks and functions;
```

```
- structural  
- dataflow  
- behavioral  
- behavioral  
  
- behavioral
```

```
endmodule
```

Example - 4-bit counter in Verilog

```
module tflopcounter(q, clk, reset);
```

```
    output [3:0] q;
```

```
    input clk, reset;
```

```
    T_FF tff0(q[0], clk, reset);
```

```
    T_FF tff1(q[1], q[0], reset);
```

```
    T_FF tff2(q[2], q[1], reset);
```

```
    T_FF tff3(q[3], q[2], reset);
```

```
endmodule
```

**4 module
instantiations**

Example - Testbench

```
`timescale 10ns / 10ps;
```

```
module stimulus;
```

```
    reg clk;
```

```
    reg reset;
```

```
    wire [3:0] q;
```

```
    tflopcounter my_counter(q, clk, reset);
```

```
    initial
```

```
        clk = 1'b0;
```

```
    always
```

```
        #5 clk = ~clk;
```

```
    initial
```

```
    begin
```

```
        reset = 1'b1;
```

```
        #15 reset = 1'b0;
```

```
        #180 reset = 1'b1;
```

```
        #10 reset = 1'b0;
```

```
        #20 $finish;
```

```
    end
```

```
    initial
```

```
        $monitor($time, "  Output q = %d", q);
```

```
endmodule
```

**module
instantiation**

**3 initial blocks
1 always block**

Port/Parameter Declarations

```
module name(portlist);  
    port declarations;  
    parameter declarations;
```

```
    wire declarations;  
    reg declarations;  
    variable declarations;
```


```
    module instantiations;  
    dataflow statements;  
    always blocks;  
    initial blocks;
```

```
    tasks and functions;
```

```
endmodule
```


Port List
 
```
module arbiter(q, a, b);  
    output [7:0] q;  
    input a;  
    inout b;  
  
endmodule
```



Port List

 
```
module arbiter(q, a, b);  
    output [7:0] q;  
    reg [7:0] q;  
    input a;  
    inout b;  
  
endmodule
```



- inputs, outputs, inouts are wires by default
- output ports can also be reg


Port List
 
```
module arbiter(  
    output reg [7:0] q,  
    input wire a,  
    inout wire b);  
  
endmodule
```



Shorthand (Verilog 2001)

Port Reg Rules

 

A and q MAY be a reg

a, b, B, Q MUST be a wire

Why is this? Hierarchy is a imaginary boundary.

In other words, q and Q, b and B, a and A are the same value.
Hence, we can have only a single storage location for a single value.

Module Parameters

- ❑ Define and use symbolic constants in the design of a module
 - The number of bits in a variable
 - The propagation delay of a gate
 - Etc ..

```
module arbiter(  
    output reg [7:0] q,  
    input wire a,  
    inout wire b);  
  
    parameter WIDTH = 32;  
    reg [WIDTH-1:0] internal;  
  
endmodule
```

Module Parameters

- ❑ Define and use symbolic constants in the design of a module
 - The number of bits in a variable
 - The propagation delay of a gate
 - Etc ..

```
module arbiter
    #(parameter WP = 8)
        (output reg [WP-1:0] q,
         input wire a,
         inout wire b);

    parameter WIDTH = 32;
    reg [WIDTH-1:0] internal;

endmodule
```

Module Instantiation and Port Matching

```
module outer_module;  
  wire [7:0] q;  
  wire a, b;
```

```
  arbiter A1(q, , b);  
endmodule
```

Positional Matching

↑
unconnected port

```
module outer_module;  
  wire [7:0] Q;  
  wire A, B;
```

```
  arbiter A1(.q(Q),  
             .b(B));  
endmodule
```

Name-based Matching

↑
unconnected port
remains unnamed

initial and always blocks

```
module name(portlist);
```

```
    port declarations;
```

```
    parameter declarations;
```

```
    wire declarations;
```

```
    reg declarations;
```

```
    variable declarations;
```

```
    module instantiations;
```

```
    dataflow statements;
```

```
    always blocks;
```

```
    initial blocks;
```

```
    tasks and functions;
```

```
endmodule
```

Initial and Always Block Statement

```
module initalways;  
reg a, b;
```

initial

begin

```
#10 a = 1;
```

```
#10 a = 0;
```

end

The begin .. end is a block statement

Statements within this block execute sequentially

The initial block is a behavioral construct

It executes a single time when $t = 0$

always

begin

```
#10 b = 1;
```

```
#10 b = 0;
```

end

The always block is a behavioral construct

It executes repeatedly


Execution of always can be controlled through
sensitivity list

```
endmodule;
```

Verilog Dataflow Modeling

Today's topic

□ Dataflow Modeling

 


Model with submodules
and gates
=
Structural

Model with always
and initial blocks
=
*Behavioral
Procedural*

Model with
assign statements
=
*Behavioral
Dataflow*

Example

 

Structural

```
module nand(q, a, b)
output q;
input a, b;

wire n;

and G1(n, a, b);
not G2(q, n);
endmodule
```

Behavioral Procedural

```
module nand(q, a, b)
output q;
reg q;
input a, b;

always @(a or b)
    q = ~(a | b);

endmodule
```

Behavioral Dataflow

```
module nand(q, a, b)
output q;
input a, b;

assign q = ~(a | b);

endmodule
```

Key differences with procedural code

- ❑ Must assign nets (wires) instead of registers

Behavioral - Procedural
assign reg

```
module nand(q, a, b)
  output q;
  reg q;
  input a, b;

  always @(a or b)
    q = ~(a | b);

endmodule
```

Procedural
Assignment

Behavioral - Dataflow
assign wire

```
module nand(q, a, b)
  output q;
  input a, b;

  assign q = ~(a | b);

endmodule
```

Continuous
Assignment

Key differences with procedural code

- ❑ Must assign nets (wires) instead of registers

Behavioral - Procedural
assign reg

```
module nand(q, a, b)
  output q;
  reg q;
  input a, b;

  always @(a or b)
    q = ~(a | b);

endmodule
```

*Any change in
a or b will cause
the always block
to re-execute*

*The procedural assignment evaluates
as a result of always block execution*

Behavioral - Dataflow
assign wire

```
module nand(q, a, b)
  output q;
  input a, b;

  assign q = ~(a | b);

endmodule
```

*Any change in
a or b will cause
the expression
to re-evaluate*

Key differences with procedural code

- ❑ Must assign nets (wires) instead of registers

Behavioral - Procedural
assign reg

```
module nand(q, a, b)
  output q;
  reg q;
  input a, b;

  always @(a or b)
    q = ~(a | b);

endmodule
```


Behavioral - Dataflow
assign wire

```
module nand(q, a, b)
  output q;
  input a, b;

  assign q = ~(a | b);

endmodule
```

 Note that both will end up as the same hardware



Key differences with procedural code

```
module wand(q, a, b, c)
  output q;
  reg q;
  input a, b;

  always @(a or b or c)
    begin
      q = a;
      q = q & b;
      q = q & c;
    end

endmodule
```

```
module wand(q, a, b, c)
  output q;
  input a, b, c;

  assign q = a;
  assign q = q & b;
  assign q = q & c;

endmodule
```

❑ And-circuit: which is correct, and which is wrong?

Key differences with procedural code

```
module chk(q, a, b, c)
output q;
reg q;
input a, b;


always @(a or b or c)
begin
q = a;
q = q & b;
q = q & c;
end

endmodule
```

```
module chk(q, a, b, c)
output q;
input a, b, c;

assign q = a;
assign q = q & b;
assign q = q & c;

endmodule
```

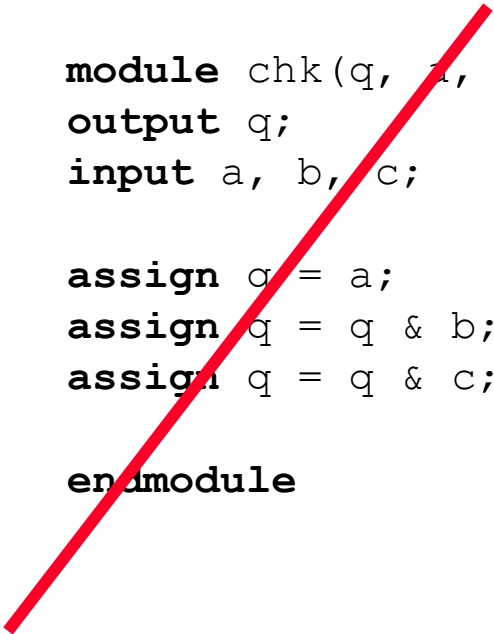


- ❑ And-circuit: which is correct, and which is wrong?
- ❑ Left hand side means three possible assignments to q, results in X (unknown)

Assign two wires

Concurrent Assign statements

```
module nand(q1, q2, a, b)
output q1, q2;
input a, b;

  assign q1 = ~(a | b);
  assign q2 = ~(a & b);
  ...
endmodule
```

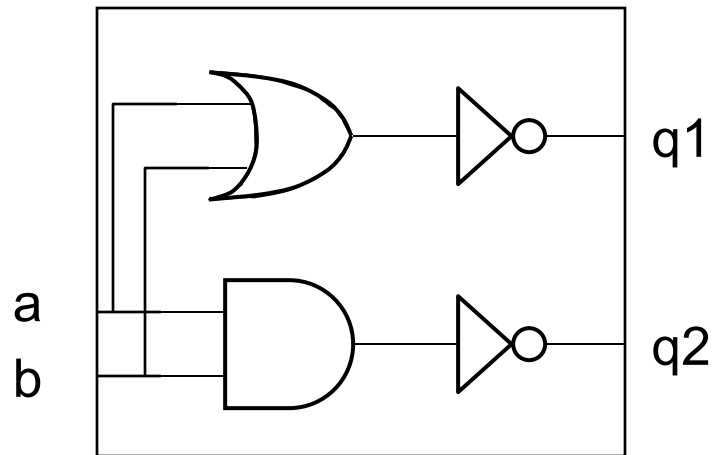


Assign two wires

Single Assign statement with a vector assignment

```
module nand(q1, q2, a, b)
  output q1, q2;
  input a, b;

  assign {q1, q2} = {~(a | b),
                    ~(a & b)};

  ...
endmodule
```

 

Useful to partition results
from an expression:

```
reg a, b, c;
wire c0, d;
assign {c0, d} = a + b + c;
```

Verilog Operators

Operand Types

```
assign {c0, d} = a + b;
```

Left-Hand Side = Right-Hand Side

nets (wire)

nets (wire)
variable (reg)
parameters
numbers
function call

Operand Bit-select and Part-select

```
wire [7:0] n;
```

<code>n[3:0]</code>	Bit 3, 2, 1, 0
---------------------	----------------

<code>n[3]</code>	Bit 3
-------------------	-------

<code>n[x]</code>	X
-------------------	---

<code>n[3+:2]</code>	Bit 3, 4
----------------------	----------

Operand Memory, Memory Indexing

```
wire [7:0] n[0:99];
```

`n[15]`

Element 16

`n[15][3]`

Bit 3 of Element 16

`n[15][0:3]`

Bits 0:3 of Element 16


`n[15:0]`

Illegal

Operand Types

Left-Hand Side = Right-Hand Side

'net' can be

 

- net
- net bit-select [n] or part-select [n:m]
- indexed net
- indexed net bit-select or part-select
- concatenated net

```
wire [7:0] n[0:99];  
{n[15][0:3], n[2]} = 12_bit_expr;
```

Operators

- ❑ Arithmetic
- ❑ Bitwise
- ❑ Reduction
- ❑ Logical
- ❑ Relational
- ❑ Shift
- ❑ Selection
- ❑ Concatenation & Replication

*We will only discuss
Verilog-specific
Operators*

General Rules for Arithmetic Precision

- ❑ Assignments will not loose precision if the target is large enough
 - If a and b are 15 bit, and c is 16 bit, then $c = a + b$ will not loose precision
- ❑ Assignments will loose precision if the target is not large enough
 - If a and b are 15 bit, and c is 8 bit, then $c = a + b$ captures the 8 lsb of the addition
- ❑ Standalone expressions *may* loose precision
 - If a and b are 15 bit, then the standalone expression $a + b$ uses 15 bit (max wordlength over a and b), and thus may loose precision
 - Standalone expressions occur in some system calls like e.g. `$display("a+b=%h", a+b);`

Reduction Operator

- ❑ Condense all bits from a vector into a single bit using a specified logical operation

```
assign q1 = &a;    // reduction-and
assign q2 = |b;    // reduction-or
assign q3 = ^c;    // reduction-xor
assign q4 = ~&d;   // reduction-nand
assign q5 = ~|e;   // reduction-nor
assign q6 = ~^f;   // reduction-xor
```

- ❑ Similar to an N-input gate of the specified type, where N equals the wordlength of the operand

- ❑ Examples

- `| (4'b0001) =`
- `^ (4'b0111) =`
- `~| (2'b11) =`
- `& (2'b1x) =`

Reduction Operator

- ❑ Condense all bits from a vector into a single bit using a specified logical operation


```
assign q1 = &a;    // reduction-and
assign q2 = |b;    // reduction-or
assign q3 = ^c;    // reduction-xor
assign q4 = ~&d;   // reduction-nand
assign q5 = ~|e;   // reduction-nor
assign q6 = ~^f;   // reduction-xor
```

- ❑ Similar to an N-input gate of the specified type, where N equals the wordlength of the operand

❑ Examples

- `| (4'b0001) = 1`
- `^ (4'b0111) = 1`
- `~| (2'b11) = 0`
- `& (2'b1x) = x`

Selection operator

 

```
wire [7:0] d;  
wire [7:0] next_r;  
reg [7:0] r;  
  
wire c;  
  
always @(posedge clk)  
    r = next_r;  
  
assign next_r = c ? d : r;
```

Concatenation and Replication

- ❑ Form wire bundles from single wires or smaller wire bundles
 - $\{a, b[3:2], c\} = \{a, b[3], b[2], c\} = \text{a 4-bit vector}$
- ❑ Concatenation can be replicated
 - $4\{a\} = \{a, a, a, a\}$
 - $\{a, 3\{b,c\}\} = \{a, b, c, b, c, b, c\}$

Operator Precedence

!	~	+	- (unary)	highest precedence
{ }	{ { } }			
()				
**				
*	/	%		
+	-		(binary)	
<<	>>	<<<	>>>	
<	<=	>	>=	
==	!=	===	!==	
&	~&			
^	~^			
	~			
&&				
? :				
				lowest precedence

Example 1

□ Write a 3-to-1 multiplexer

- Inputs D0, D1, D2 (4-bit)
- Select input S (2-bit)
- Output Y (4-bit)

S	Y
0	D0
1	D0
2	D1
3	D2

Example 1

□ Write a 3-to-1 multiplexer

- Inputs D0, D1, D2 (4-bit)
- Select input S (2-bit)
- Output Y (4-bit)

S	Y
0	D0
1	D0
2	D1
3	D2

```
module mux(output [7:0] Y,  
           input  [1:0] S,  
           input  [7:0] D0, D1, D2);  
  
    assign Y = (S == 0) ? D0 :  
               (S == 1) ? D0 :  
               (S == 2) ? D1 : D2;  
  
endmodule
```

Example 1

□ Write a 3-to-1 multiplexer

- Inputs D0, D1, D2 (4-bit)
- Select input S (2-bit)
- Output Y (4-bit)

S	Y
0	D0
1	D0
2	D1
3	D2

```
module mux(output [7:0] Y,  
           input  [1:0] S,  
           input  [7:0] D0, D1, D2);  
  
    assign Y = (S[1]) ? ((S[0]) ? D1 : D2) : D0;  
  
endmodule
```

Example 2

- ❑ Develop an 8-bit * 8-bit multiplier with 8-bit output, reflecting the 8 msb of the multiplication

Example 2

- ❑ Develop an 8-bit * 8-bit multiplier with 8-bit output, reflecting the 8 msb of the multiplication

```
module mul(output [7:0] Y,  
           input  [7:0] D0, D1);  
  
    wire    [15:0] mul_out;  
  
    assign mul_out = D0 * D1;  
    assign Y = mul_out[15:8];  
  
endmodule
```

Example 3

- ❑ Develop a rounding module with 8-bit input and 4-bit output. The 4-bit input captures the *rounded* output of the 8 input bits. That is, if the 4 lsb of the input are bigger than 0111, then the output should be incremented.

Example 3

- ❑ Develop a rounding module with 8-bit input and 4-bit output. The 4-bit input captures the *rounded* output of the 8 input bits. That is, if the 4 lsb of the input are bigger than 0111, then the output should be incremented.

Rounding Trick: Add 1/2 lsb

1001	1100	8-bit input
0000	1000	add 1/2 lsb of 4-bit output
1010		4-bit output

Example 3

- Develop a rounding module with 8-bit input and 4-bit output. The 4-bit input captures the *rounded* output of the 8 input bits. That is, if the 4 lsb of the input are bigger than 0111, then the output should be incremented.

```
module round(output [3:0] Y,  
             input  [7:0] D);  
  
    wire [7:0] A;  
  
    assign A = D + 4'b1000;  
    assign Y = A[7:4];  
  
endmodule
```

Example 4

- ❑ Develop a multiply-accumulate module with 40-bit accumulator and 2x16-bit inputs. The accumulator register is triggered on pos clock edge and has a negative asynchronous reset.

Example 4

- ❑ Develop a multiply-accumulate module with 40-bit accumulator and 2x16-bit inputs. The accumulator register is triggered on pos clock edge and has a negative asynchronous reset.

```
module mac(output reg [39:0] Y,  
           input          clk, rst,  
           input [15:0]    D0, D1);  
  
    wire    [39:0] next_Y;  
  
    always @(posedge clk or negedge rst)  
        Y = (rst) ? next_Y : 0;  
  
    assign next_Y = Y + (D0 * D1);  
  
endmodule
```

Example 5

- ❑ Design a programmable shifter that will shift an 8-bit word over 0 .. 3 positions to the right, inserting zeroes at the msb side

Example 5

- Design a programmable shifter that will shift an 8-bit word over 0 .. 3 positions to the right, inserting zeroes at the msb side

```
module shft(output [7:0] Y,  
            input  [1:0] s,  
            input  [7:0] a);  
  
    assign Y = (s == 2'b11) ? (a << 3) :  
                (s == 2'b10) ? (a << 2) :  
                (s == 2'b01) ? (a << 1) :  
                a;  
  
endmodule
```


Example 5

- Design a programmable shifter that will shift an 8-bit word over 0 .. 3 positions to the right, inserting zeroes at the msb side

```
module shft(output [7:0] Y,  
            input  [1:0] s,  
            input  [7:0] a);  
    wire [7:0] Y1;  
  
    assign Y1 = (s[0]) ? (a >> 1) : a;  
    assign Y   = (s[1]) ? (Y1 >> 1) : Y1;  
  
endmodule
```

Example 5

- Design a programmable shifter that will shift an 8-bit word over 0 .. 3 positions to the right, inserting zeroes at the msb side

```
module shft(output [7:0] Y,  
            input  [1:0] s,  
            input  [7:0] a);  
    wire [7:0] Y1;  
  
    assign Y1 = (s[0]) ? {1'b0,a[7:1]} : a;  
    assign Y   = (s[1]) ? {1'b0,Y1[7:1]} : Y1;  
  
endmodule
```


Verilog Multiplexed Datapaths

Multiplexed Datapaths - Disclaimer

- ❑ We will cover very specific Verilog modeling guidelines to build hardware modules called 'multiplexed datapaths'
- ❑ Not the only way to build hardware in Verilog
 - We will see other 'design methods' later
- ❑ But, if you use the 'multiplexed datapath' method, you **MUST** stick to the following guidelines

What is a multiplexed datapath ?

 - ❑ A module with a single clk and rst input
- ❑ Zero or more inputs, one or more outputs
- ❑ Edge-triggered flip-flops
- ❑ Outputs depend *only* on registers



Why single-clock ?

- ❑ A module with a single clk and rst input
- ❑ Zero or more inputs, one or more outputs
- ❑ Edge-triggered flip-flops
- ❑ Outputs depend *only* on registers

Simplifies generation and distribution of clock signal
in the implementation

Why edge-triggered flip-flops ?


- ❑ A module with a single clk and rst input
- ❑ Zero or more inputs, one or more outputs
- ❑ Edge-triggered flip-flops
- ❑ Outputs depend *only* on registers

A single type of storage module simplifies test
A single type of reset signal simplifies initialization

Why outputs depend only on registers ?


- ❑ A module with a single clk and rst input
- ❑ Zero or more inputs, one or more outputs
- ❑ Edge-triggered flip-flops
- ❑ Outputs depend *only* on registers

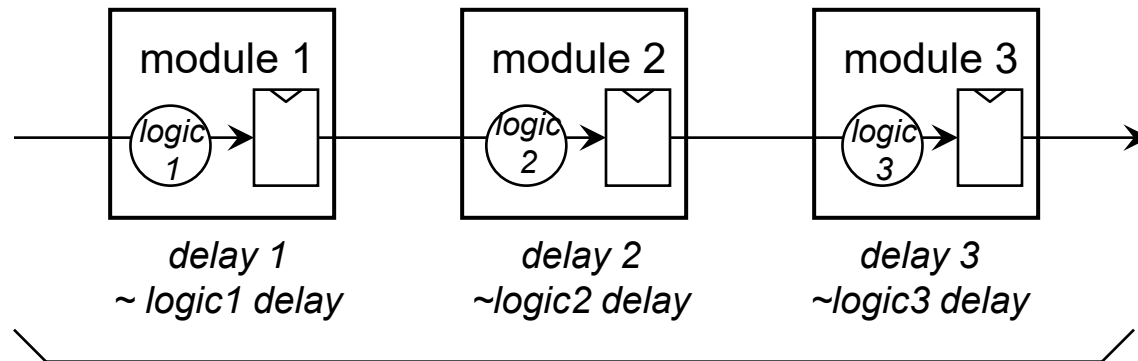Make sure that system-level delay, i.e. critical path, is just $\max(\text{module-level delay})$, not $\text{sum}(\text{module-level delay})$




$$\text{System Delay} = \max(\text{delay1}, \text{delay2}, \text{delay3}) + \text{routing_delay}$$

Template for a Multiplexed Datapath

 


How to model an edge-triggered register
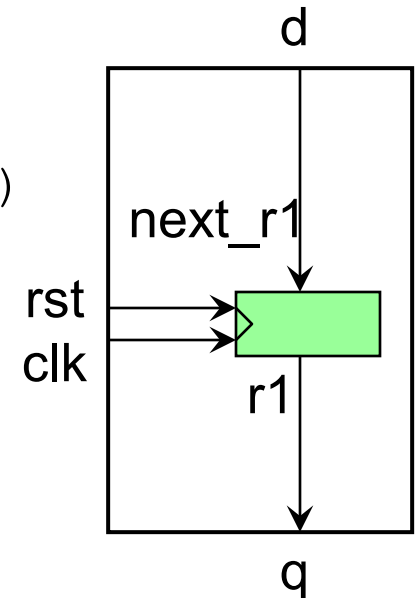
```
module a_module(output wire q,  
                input wire rst,  
                input wire clk,  
                input wire d);  
  
  wire next_r1;  
  reg   r1;  
  
  always @(posedge clk or negedge rst)  
    if (rst)  
      r1 = next_r1;  
    else  
      r1 = 0;  
  
  assign next_r1 = d;  
  assign q = r1;  
endmodule
```



How to model an edge-triggered register

 
```
module a_module(output wire q,  
                input wire rst,  
                input wire clk,  
                input wire d);  
  
    wire next_r1;  
    reg  r1;  
  
    always @(posedge clk or negedge rst)  
        if (rst)  
            r1 = next_r1;  
        else  
            r1 = 0;  
  
    assign next_r1 = d;  
    assign q = next_r1;  
endmodule
```



No!


How to model two edge-triggered registers

```
module a_module(output wire q,  
                input wire rst,  
                input wire clk,  
                input wire d);  
  
    wire next_r1, next_r2;  
    reg  r1, r2;  
  
    always @(posedge clk or negedge rst) rst  
        if (rst) begin  
            r1 = next_r1;  
            r2 = next_r2;  
        end else begin  
            r1 = 0;  
            r2 = 0;  
        end  
    end  
    assign next_r1 = d;  
    assign next_r2 = r1;  
    assign q = r2;  
endmodule
```

 

How to model two edge-triggered registers


```
module a_module(output wire q,  
                input wire rst,  
                input wire clk,  
                input wire d);  
  
    wire next_r1, next_r2;  
    reg  r1, r2;  
  
    always @(posedge clk or negedge rst)  
        if (rst) begin  
            r1 = next_r1;  
            r2 = next_r2;  
        end else begin  
            r1 = 0;  
            r2 = 0;  
        end  
  
    assign next_r1 = d;  
    assign next_r2 = r1;  
    assign q = r2;  
endmodule
```

 

Will leave out drawing of clk net
and rst net from now

Add two inputs, capture in a register
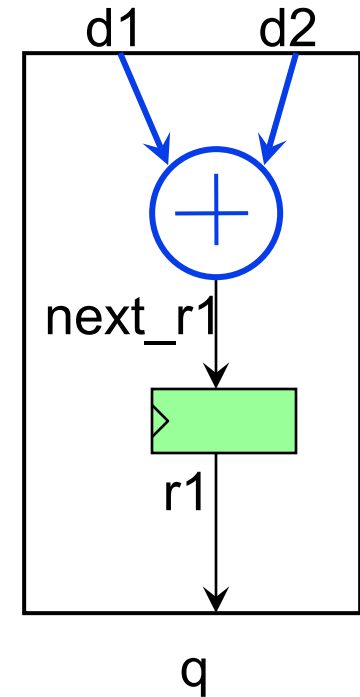
```
module a_module(output wire q,  
                input wire rst,  
                input wire clk,  
                input wire d1, d2);  
  
    wire next_r1;  
    reg r1;  
  
    always @(posedge clk or negedge rst)  
        if (rst)  
            r1 = next_r1;  
        else  
            r1 = 0;  
  
    assign next_r1 = d1 + d2;  
    assign q = r1;  
endmodule
```




Take a close look at the addition

```
input d1, d2;
```


```
wire next_r1;
```

```
assign next_r1 = d1 + d2;
```

 

How to get the carry bit ?
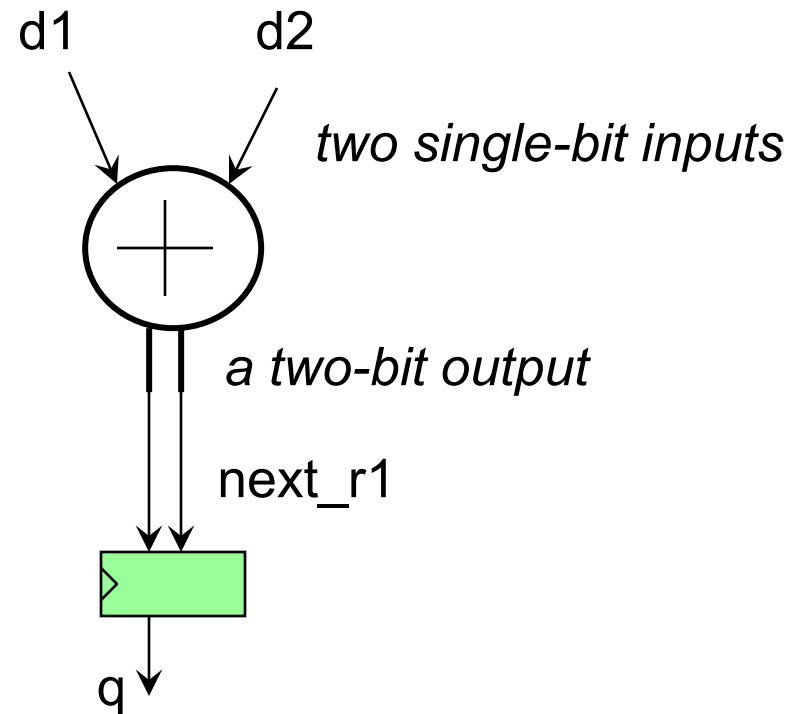
```
input d1, d2;  
wire [1:0] next_r1;  
reg [1:0] r1;  
  
assign next_r1 = d1 + d2;  
assign q = r1[1];
```




Not so good, will require a two-bit register

Better solution


```
module a_module(output wire q,  
                input wire rst,  
                input wire clk,  
                input wire d1, d2);  
  
    wire next_r1;  
    reg  r1;  
    wire dummy;  
  
    always @(posedge clk or negedge rst)  
        if (rst)  
            r1 = next_r1;  
        else  
            r1 = 0;  
  
    assign {next_r1, dummy} = d1 + d2;  
    assign q = r1;  
endmodule
```

How to model an multiplexed register

 
```
module a_module(output wire q,  
                input wire rst,  
                input wire clk,  
                input wire d, c);  
  
    wire next_r1;  
    reg r1;  
  
    always @(posedge clk or negedge rst)  
        if (rst)  
            r1 = next_r1;  
        else  
            r1 = 0;  
  
    assign next_r1 = c ? d : r1;  
    assign q = r1;  
endmodule
```



Multiplexer allows controlled update

 


 - ❑ Eg. *d* is only valid once every three clock cycles
- ❑ Capture *d* in register only when *c* = 1
- ❑ Otherwise, retain value of *q*
- ❑ *c* is a 'logical' clock signal (in contrast to the physical clock signal *clk*)




Muxed registers are key to Muxed Datapath

Overall Idea

 


 
One clock cycle
3 Multiplier
2 Adders (2-input)





Three clock cycles
1 Multiplier
1 Adder
 n Multiplexers

Muxed registers are key to Muxed Datapath


Overall Idea

  

AREA
TIME
TRADEOFF

  


Let's try this

 


```
module vecmul(q, rst, clk, in1, in2, in3);  
    output [7:0] q;  
    input rst, rst;  
    input [7:0] in1, in2, in3;  
    parameter c1 = 8'd2;  
    parameter c2 = 8'd4;  
    parameter c3 = 8'd6;  
  
    wire next_r1;  
    reg r1;  
  
    always @(posedge clk or negedge rst)  
        if (rst)  
            r1 = next_r1;  
        else  
            r1 = 0;  
  
    assign next_r1 = c1 * in1 +  
                    c2 * in2 +  
                    c3 * in3;  
  
    assign q = r1;  
endmodule
```

 Now, we reduce the number of *, + operations



```
module vecmul(q, rst, clk, in1, in2, in3);  
    output [7:0] q;  
    input rst, rst;  
    input [7:0] in1, in2, in3;  
    parameter c1 = 8'd20;  
    parameter c2 = 8'd40;  
    parameter c3 = 8'd60;  
  
    wire next_r1;  
    reg r1;  
  
    wire [7:0] m1, m2;  
    wire [10:0] a1, a2, aq; // 16-bit worst case  
  
    assign aq = a2 + a1;  
    assign a1 = m1 * m2;  
  
endmodule
```

Add muxes on m1, m2. Add control input.

 

```
module vecmul(q, rst, clk, in1, in2, in3, step);
    output [7:0] q;
    input rst, rst;
    input [7:0] in1, in2, in3;
    input [1:0] step;
    parameter c1 = 8'd20;
    parameter c2 = 8'd40;
    parameter c3 = 8'd60;

    wire next_r1;
    reg r1;


    wire [7:0] m1, m2;
    wire [10:0] a1, a2, aq; // 16-bit worst case

    assign aq = a2 + a1;
    assign a1 = m1 * m2;
    assign m1 = (step == 0) ? c1 :
                (step == 1) ? c2 : c3;
    assign m2 = (step == 0) ? in1 :
                (step == 1) ? in2 : in3;

endmodule
```

step is a control input

Add muxes on a2. Add accumulator reg.

 

```
module vecmul(q, rst, clk, in1, in2, in3, step);
    output [7:0] q;
    input rst, rst;
    input [7:0] in1, in2, in3;
    input [1:0] step;
    parameter c1 = 8'd20;
    parameter c2 = 8'd40;
    parameter c3 = 8'd60;


    wire next_r1;
    reg r1;

    wire [7:0] m1, m2;
    wire [10:0] a1, a2, aq; // 16-bit worst case
    reg [10:0] aq_reg;

    always @(posedge clk) aq_reg = aq;

    assign aq = a2 + a1;
    assign a1 = m1 * m2;
    assign m1 = (step == 0) ? c1 :
                (step == 1) ? c2 : c3;
    assign m2 = (step == 0) ? in1 :
                (step == 1) ? in2 : in3;
    assign a2 = (step == 0) ? 0 : aq_reg;
endmodule
```

System Interconnect.

 

```

module vecmul(q, rst, clk, in1, in2, in3, step);
    output [7:0] q;
    input rst, rst;
    input [7:0] in1, in2, in3;
    input [1:0] step;
    parameter c1 = 8'd20;
    parameter c2 = 8'd40;
    parameter c3 = 8'd60;

    wire next_r1;
    reg r1;


    wire [7:0] m1, m2;
    wire [10:0] a1, a2, aq; // 16-bit worst case
    reg [10:0] aq_reg;

    always @(posedge clk) aq_reg = aq;

    assign aq = a2 + a1;
    assign a1 = m1 * m2;
    assign m1 = (step == 0) ? c1 :
                (step == 1) ? c2 : c3;
    assign m2 = (step == 0) ? in1 :
                (step == 1) ? in2 : in3;
    assign a2 = (step == 0) ? 0 : aq_reg;
    assign q = aq_reg;
endmodule

```

Simple Optimizations

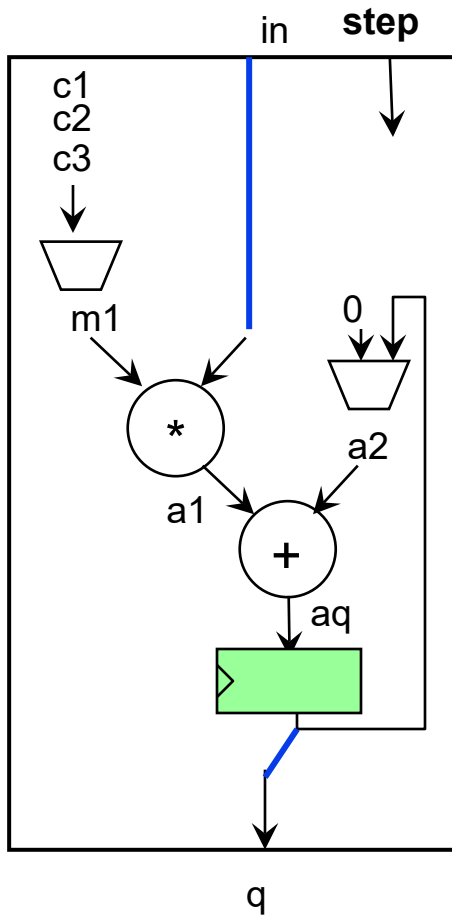

```
module vecmul(q, rst, clk, in, step);
    output [7:0] q;
    input rst, rst;
    input [7:0] in;
    input [1:0] step;
    parameter c1 = 8'd20;
    parameter c2 = 8'd40;
    parameter c3 = 8'd60;

    wire next_r1;
    reg r1;


    wire [7:0] m1;
    wire [10:0] a1, a2, aq; // 16-bit worst case
    reg [10:0] aq_reg;

    always @(posedge clk) aq_reg = aq;

    assign aq = a2 + a1;
    assign a1 = m1 * in;
    assign m1 = (step == 0) ? c1 :
                (step == 1) ? c2 : c3;
    assign a2 = (step == 0) ? 0 : aq_reg;
    assign q = aq_reg;
endmodule
```

Input is now sequential: in1, in2, in3 can share an input port

Result of 'Muxed Datapath'

 


Verilog FSM-based Control


Finite State Machine Template

□ Sequential Machine defined by

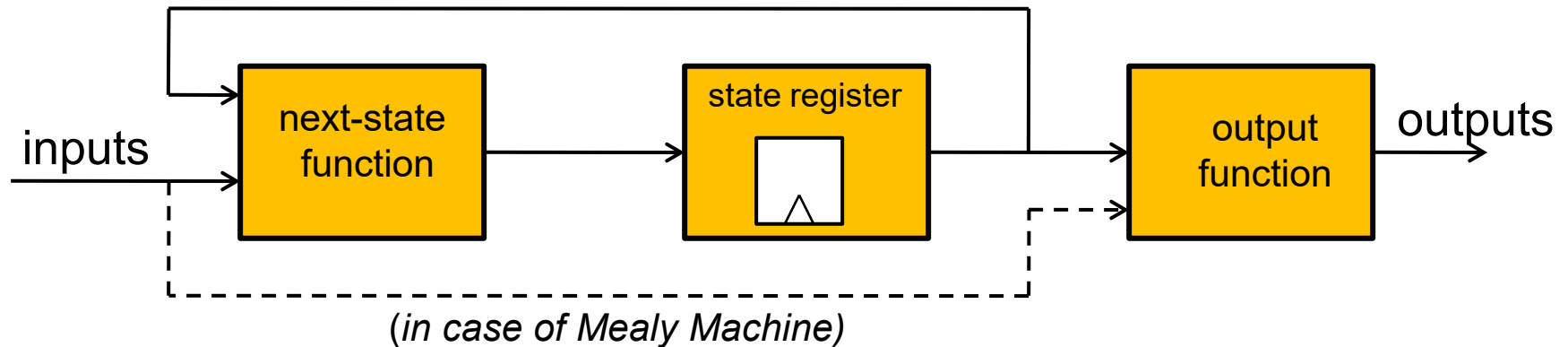
- Set of Inputs and Outputs
- Set of States
- Initial State (reset function)
- State Transitions




Design Process

 

Design Process

 


Design Process

 

Design Process


We will
focus on
and

 

 Example FSM Design

- ❑ Create an FSM that turns the first '1' of a string of consecutive '1' into a '0'.

Each clock cycle, a new input is provided



Example FSM Design


□ How many states?

Input	1	0	1	0	0	0	1	1	1	0	0	1	1	1	1	1	1	1
Output	0	0	0	0	0	0	0	1	1	0	0	0	1	1	1	1	1	1

Example FSM Design

□ How many states?

Input	1	0	1	0	0	0	1	1	1	0	0	1	1	1	1	1	1	1
Output	0	0	0	0	0	0	0	1	1	0	0	0	1	1	1	1	1	1

 

Example FSM Design

□ How many states?

Input	1	0	1	0	0	0	1	1	1	0	0	1	1	1	1	1	1	1
Output	0	0	0	0	0	0	0	1	1	0	0	0	1	1	1	1	1	1

S0


S1

S2

Example FSM Design

□ How many states?

Input	1	0	1	0	0	0	1	1	1	0	0	1	1	1	1	1	1	1
Output	0	0	0	0	0	0	0	1	1	0	0	0	1	1	1	1	1	1

 

output
S0 -> 0
S1 -> 0
S2 -> 1

Verilog Mapping of FSM - Generic Ideas

- ❑ Use 'parameter' to express state encoding


```
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;
```

- ❑ This is a *symbolic* encoding, not necessarily the encoding that will be used by the synthesis tool
- ❑ Use standard conventions for coding logic
 - Use non-blocking <= for registers, specify correct reset and edge-triggered behavior
 - Use blocking = for combinational logic, make sure sensitivity lists are complete

 Example FSM Design - Verilog Mapping I

```
module fsm(q, i, clk, rst);
  input i, clk, rst;
  output q;
  reg q;
  reg [1:0] state;
  parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;


  always @(posedge clk or posedge rst)
    if (rst) begin
      state <= s0; q <= 1'b0;
    end else begin
      case (state)
        s0: if (i == 1'b1) begin
              state <= s1;
              q <= 1'b0;
            end else begin
              state <= s0;
              q <= 1'b0;
            end
        s1: ..
        s2: ..
      endcase
    end
end
endmodule
```



output
S0 -> 0
S1 -> 0
S2 -> 1

 Example FSM Design - Verilog Mapping I

- ❑ One single always block
 - Next-state logic and state update in same block
 - Output will always have a register




Example FSM Design - Verilog Mapping II

```
reg q;  
reg [1:0] state;  
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;
```

```
always @(posedge clk or posedge rst)  
  if (rst)  
    state <= s0;  
  else  
    case (state)  
      s0: if (i == 1'b1)  
          state <= s1;  
          else  
            state <= s0;  
      s1: ..  
    endcase
```

```
always @(state)  
  q = 1'b0;    // default assignment  
  case (state)  
    s0: q = 1'b0;  
    s1: q = 1'b0;  
    s2: q = 1'b1;  
  endcase
```

```
endmodule
```

 


output
S0 -> 0
S1 -> 0
S2 -> 1

 Example FSM Design - Verilog Mapping II

❑ Two always block

- Next-state logic and state update in same block
- Output can be combinational




Example FSM Design - Verilog Mapping III

```
reg q;  
reg [1:0] state, next_state;  
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;
```

```
always @(posedge clk or posedge rst)  
  if (rst)  
    state <= s0;  
  else  
    state <= next_state;
```

```
always @(state or i) begin  
  // next state encoding  
  next_state = s0;  
  case (state)  
    s0: if (i == 1'b1)  
          next_state = s1;  
        else  
          next_state = s0;  
    s1: ..  
  endcase  
end
```
 
```
always @(state)  
  // output encoding  
endmodule
```




output
S0 -> 0
S1 -> 0
S2 -> 1

 Example FSM Design - Verilog Mapping III

❑ Three always block

- Next-state logic and state update in same block
- Output can be combinational



One, two, three always block

	1 always block	2 always block	3 always block	
Combinational Output		✓	✓	
State Update separate from next-state Logic			✓	