

4-Bit MULTIPLY

$$\begin{array}{r}
 a \quad 1011 \\
 b \quad 1101 \\
 \hline
 \end{array}$$

$$\begin{array}{r}
 11011 \\
 00000 \\
 10011 \\
 10101 \\
 10011 \\
 \hline
 10001111
 \end{array}$$

$$b[0] = 1$$

$$b[1] = 0$$

$$b[2] = 1$$

$$b[3] = 1$$

```
module mymult2(input wire      clk,
               input wire      reset,
               input wire [15:0] a,
               input wire [15:0] b,
               input wire      start,
               output wire [31:0] result,
               output wire      done);
```

```
(* multstyle = "logic" *) reg [31:0] r, next_r;
reg                               d, next_d;
```

```
always @(posedge clk)
begin
    r <= (reset) ? 32'h0 : next_r;
    d <= (reset) ? 1'b0 : next_d;
end
```

```
// IMPLEMENTATION 2
```

```
reg [31:0] tmp[15:0]; - PARTIAL PRODUCT ACCUMULATOR
reg [31:0] tmpa;      - SHIFTED VERSION OF A
```

```
integer    j;
```

```
always @(*)
```

```
begin
```

```
    tmp[0] = b[0] ? {16'b0, a} : 32'b0;
```

```
    for (j = 1; j < 16; j = j + 1)
```

```
    begin
```

```
        tmpa = {15'b0, a} << j;
```

```
        tmp[j] = tmp[j-1] + (b[j] ? tmpa : 32'b0);
```

```
    end
```

```
    next_r = tmp[15];
```


```
    next_d = start;
```

```
end
```

```
assign result = r;
```

```
assign done   = d;
```


```
endmodule
```

 

```

module mymult1(input wire      clk,
               input wire      reset,
               input wire [15:0] a,
               input wire [15:0] b,
               input wire      start,
               output wire [31:0] result,
               output wire      done);

```

 

```

(* multstyle = "logic" *) reg [31:0] r, next_r;
reg                        d, next_d;

```

```

always @(posedge clk)
begin
    r <= (reset) ? 32'h0 : next_r;
    d <= (reset) ? 1'd0 : next_d;
end

```

```

// IMPLEMENTATION 1
always @(*)
begin
    next_r = {16'b0,a} * {16'b0,b};
    next_d = start;
end

```

```

assign done    = d;
assign result  = r;

```

```

endmodule

```

